

# COMPOSITE - TO - TTL ADAPTOR FOR MONOCHROME MONITORS

Among the welcome side-effects of the current invasion of IBM PCs and compatibles are the drastic price cuts for high-resolution, 12 and 14 inch, TTL-compatible monochrome monitors. The circuit described here makes it possible to use such a display in conjunction with a computer that has a composite video output only.

Many owners of popular home computers must at some time have been envious of IBM PC users, because these are in a position to look at text and graphics on a restive, high-resolution, non-glare monitor instead of on a (modified) TV set tuned to channel 36, and barely capable of displaying 80 characters per line. Until recently, however, the cost of a TTL monitor was such that manufacturers of home computers in the lower price ranges did not even consider equipping these with a digital output. The inexpensive adaptor circuit described here should allow many owners of the first generation of home computers to benefit from the advantages offered by the TTL-compatible monitor.

## Circuit description

The circuit shown in Fig. 1 effectively splits the CVBS (composite video-blanking-synchronisation) signal applied to the input into three components: horizontal and vertical synchronization pulses, and video. These three signals are then converted to digital level to enable driving the corresponding inputs on the TTL monitor.

The low reference level of the CVBS signal is first set to 0 V by an active clamping circuit around IC<sub>1</sub>. Figure 2 shows the voltage levels in a CVBS signal. Note that the amplitude of  $U_{\text{sync}}$  is usually about one third of that of  $U_{\text{video}}$ . The switching threshold of comparator IC<sub>2</sub> is set such that only the synchronization pulses can cause the opamp output to go low. The composite sync signal is then fed to XOR gate N<sub>1</sub> and to a two-section R-L-C low-pass filter. Switch S<sub>1</sub> connected to pin 2 of N<sub>1</sub> selects the signal polarity at the H-sync output. The presence there of V-sync pulses has no consequence for the TTL monitor. The V-sync pulses obtained after filtering in the low-pass can be inverted, if necessary, by closing S<sub>2</sub>. Inversion is probably not necessary for most types of monitor, but users are well advised to consult the relevant manual in case of doubt.

A fast comparator, based around opamp Type 733 (IC<sub>3</sub>) and FETs T<sub>1</sub>-T<sub>2</sub>, extracts the video component from the CVBS input signal. It should be noted that the attainable contrast ratio is mainly determined by the speed of the opamp, so that the circuit does not work correctly if IC<sub>3</sub> is replaced by a slower type. The toggle point of IC<sub>3</sub> is set to the average video level by P<sub>2</sub>. Impedance conversion between the opamp and the digital video input of the monitor is achieved with T<sub>4</sub> and T<sub>5</sub>, the latter functioning as an adjustable zener diode.

## Construction, setting up and application

The adaptor is constructed on the printed circuit board shown in Fig. 3. The two inductors are preferably ferrite-

encapsulated radial types from Toko. The completed unit can be installed in the monitor, which usually has room to spare inside. This has the advantage that the adaptor can be fed from the existing power supply, ensuring correct interface levels (check the specification of the monitor in this respect). As shown in the circuit diagram, the adaptor is uncritical of the supply voltage level, as long as this is between 5 and 12 V, and well regulated.

An oscilloscope enables the unit to be aligned quickly. With reference to Figs. 2 and 3, measure the levels  $\frac{1}{2}U_{\text{sync}}$  (x), and  $U_{\text{sync}} + \frac{1}{2}U_{\text{video}}$  (y), and set these voltages as the toggle levels for IC<sub>2</sub> (P<sub>1</sub>) and IC<sub>3</sub> (P<sub>2</sub>) respectively. Adjust P<sub>3</sub> for optimum picture resolution and stability. When an oscilloscope is not available, set P<sub>2</sub> and P<sub>3</sub> to the centre of

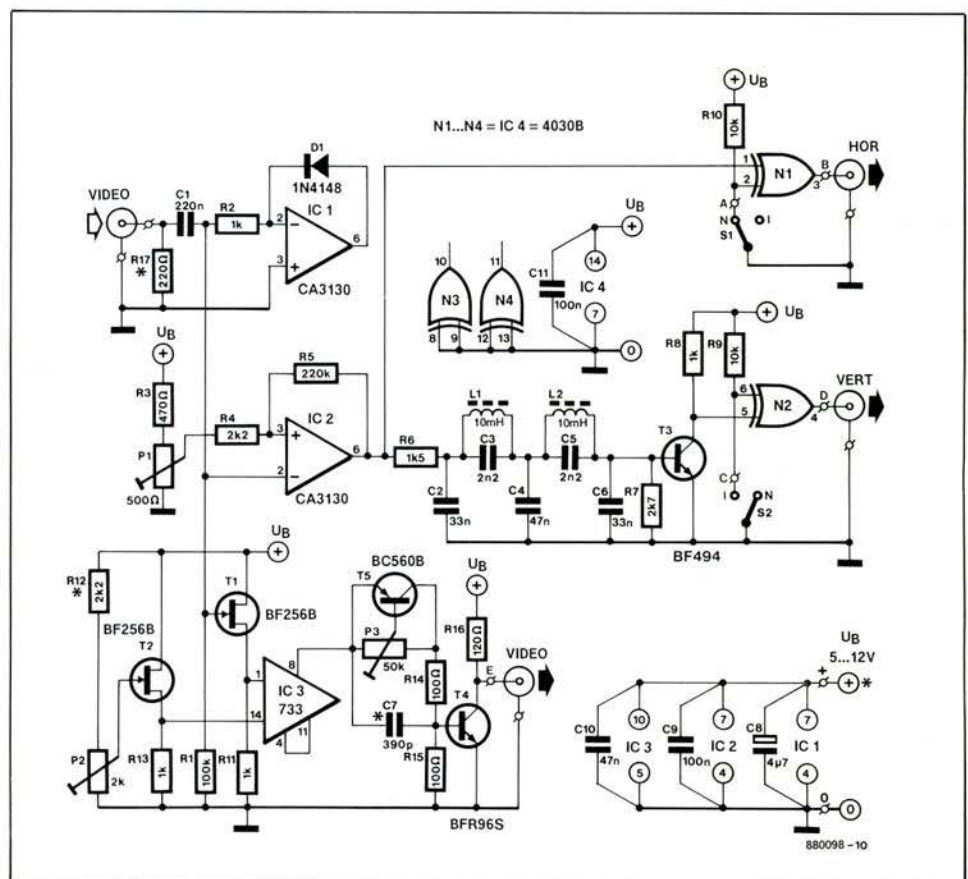


Fig. 1. Circuit diagram of the composite-to-TTL converter.



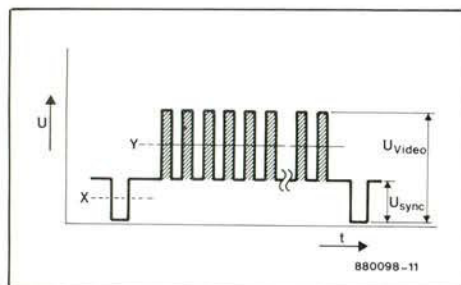


Fig. 2. Toggle level for the sync comparator (X) and for the video comparator (Y).


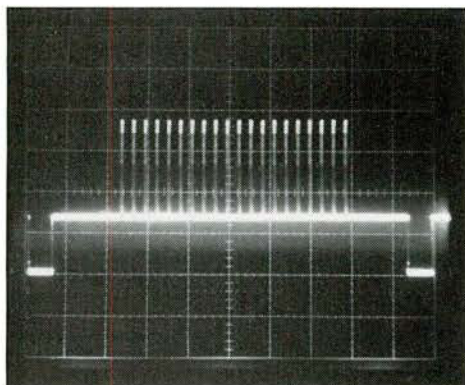
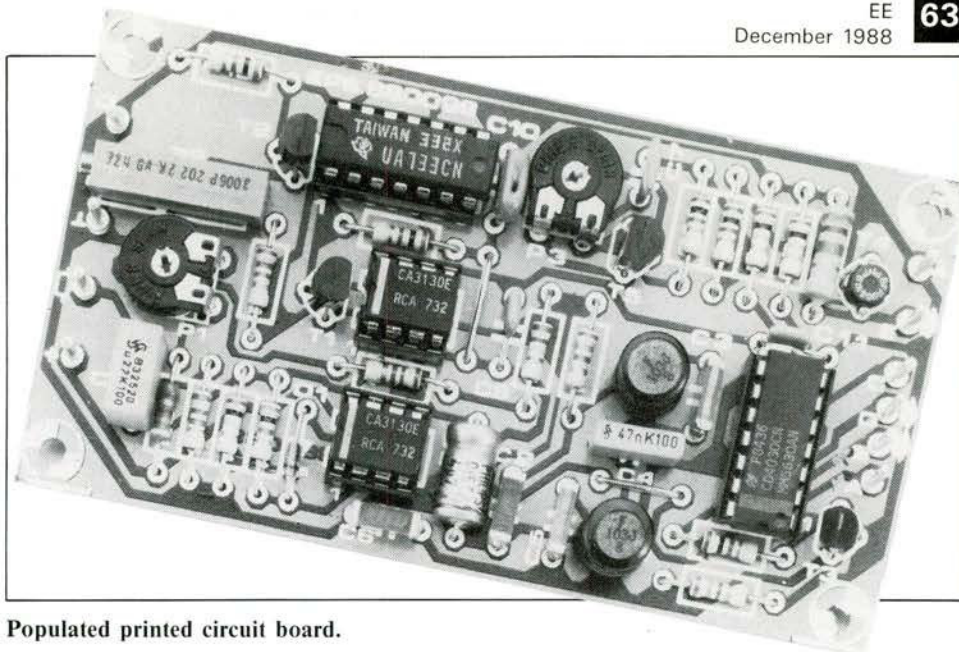


Fig. 3. Oscilloscope display of one line of text in a monochrome CVBS signal supplied by a BBC model B computer.

their travel, and turn the wiper of  $P_1$  to ground. Apply the input signal, and carefully advance  $P_1$  until the picture synchronizes. Then adjust the other two presets for optimum picture quality, first  $P_2$  and then  $P_3$ .

The circuit is dimensioned to work with input video levels between  $1 V_{pp}$  and  $4 V_{pp}$ . The value of  $R_{17}$  may have to be increased, or the resistor may have to be omitted, to ensure correct operation with home computers whose output level is lower than  $1 V_{pp}$ . Signal levels exceeding  $4 V_{pp}$  can be accommodated by lowering the value of  $R_{12}$ . Capacitor  $C_7$ , finally, also allows some experimenting because it may not be required unless a very high resolution monitor ( $>80$  characters per line) is being used.

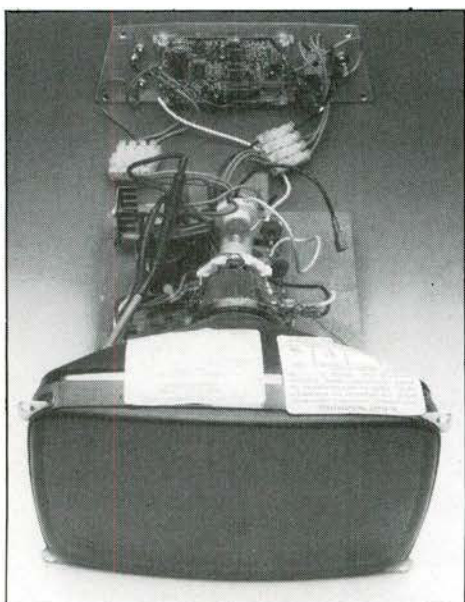

Populated printed circuit board.

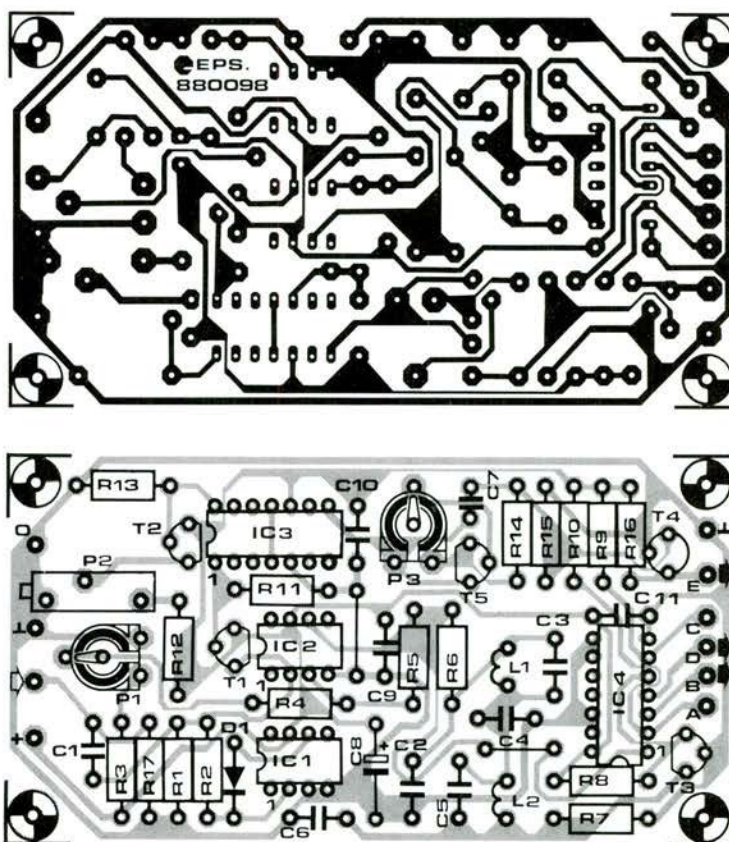


Fig. 4. Printed circuit board for the adaptor.

#### Parts list

##### Resistors ( $\pm 5\%$ ):

$R_1 = 100K$   
 $R_2; R_8; R_{11}; R_{13} = 1K\Omega$   
 $R_3 = 470R$   
 $R_4; R_{12} = 2K\Omega$   
 $R_5 = 220K$   
 $R_6 = 1K5$   
 $R_7 = 2K7$   
 $R_9; R_{10} = 10K$   
 $R_{14}; R_{15} = 100R$   
 $R_{16} = 120R$   
 $R_{17} = 220R$   
 $P_1 = 500R$  preset H  
 $P_2 = 2K$  or  $2K5$  multiturn preset  
 $P_3 = 50K$  preset H

##### Capacitors:

$C_1 = 220n$   
 $C_2; C_6 = 33n$   
 $C_3; C_5 = 2n2$   
 $C_4; C_{10} = 47n$   
 $C_7 = 390p$   
 $C_8 = 4\mu 7; 16 V$   
 $C_9; C_{11} = 100n$

##### Semiconductors:

$D_1 = 1N4148$   
 $T_1; T_2 = BF256B$   
 $T_3 = BF494$   
 $T_4 = BFR96S$  (listed by Bonex Ltd.)  
 $T_5 = BC560B$

$IC_1; IC_2 = CA3130$

$IC_3 = \mu A733$  or  $LM733$

$IC_4 = CD4030B$

##### Miscellaneous:

$L_1; L_2 = 10mH$  radial inductor, e.g. Toko Type 181LY-103 (Circuit stock no. 34-10302).  
 $S_1; S_2 =$  miniature SPST switch.  
 PCB Type 880098 (see Readers Services page).