



Extra amplification is desirable in almost every extended video chain. We are talking about, for example, compensating for losses in cables, strengthening the signal from a not very sensitive input, or other applications where signal levels have to be tuned in to each other.

This simple amplifier is ideal for all these applications. Furthermore it also acts as a distributor as it is equipped with three outputs as standard.

# video amplifier

universal  
amplifier and  
distributor  
for video  
signals

A video amplifier rarely needs a high gain. By 'high' we mean a factor of 100 or more, as is the norm for audio pre-amplifiers. For adjusting video levels a gain factor of 2 or 3 times is generally called for – maybe a bit more in a few cases.

In this circuit we have made the amplification adjustable between 1 x and a good 4 x, so that the amplifier is suitable for almost any situation where boosting is needed. The maximum output voltage is 4 V<sub>pp</sub>, and the input and output impedance is, of course, set at 75 ohms.

As well as being a normal amplifier, this circuit can also be used as a video signal distributor, which is handy if more than one channel in a video chain are to be driven from one video signal. As we have already said, the amplifier has three outputs. However, that is not to say that they all have to be used. The circuit can also be used with just one or two outputs.

Now the only data needed to complete the technical specification of the amplifier is the bandwidth. This is at least 5 MHz providing the specified semiconductors are used.

## The circuit diagram

A good video amplifier need not be very

complicated, as is shown by figure 1a. The circuit contains a very ordinary two-stage amplifier (T1/T2) followed by an emitter follower. The transistors used are simply normal BC and BD types because these can quite easily fulfil the required conditions for adequate bandwidth. A nice side-effect is, of course, that these transistors are relatively cheap, and in this case expensive HF types are simply not needed.

The input impedance is set to 75 ohms by R1. The signal travels from the input via C2 to the base of T1. Because the content of the video signal can change a lot, the d.c. current setting of T1 is provided by a small circuit (R3, P1, C1, R2 and D1). The maximum output voltage swing of the amplifier can be set using P1. We will deal with setting this potentiometer later. The base of transistor T2 is connected directly to the collector of T1 thus forming a direct coupled amplifier, the amplification of which can be varied with potentiometer P2 in the feedback network. The amplification factor is defined by the ratio between R5 and the resistance of the R6/R7/P2/C3 network. With the values we have used, P2 covers a range of 1.95 x to 8.7 x. With the





12-37

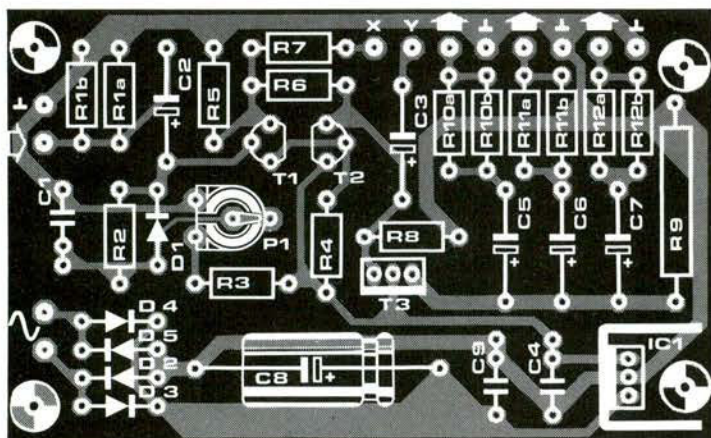
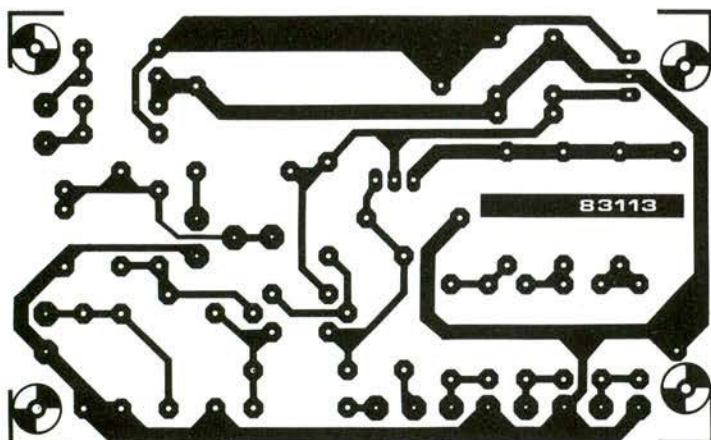


Figure 2. The printed circuit board contains both the amplifier and power supply. Only the mains transformer is not mounted on the board.

#### Parts list

##### Resistors:

R1, R10 ... R12 = 75  $\Omega$  \*  
 R2 = 10 k  
 R3 = 8k2  
 R4 = 1 k  
 R5, R7 = 180  $\Omega$   
 R6 = 3k3  
 R8 = 470  $\Omega$   
 R9 = 56  $\Omega$ /5 W\*\*  
 P1 = 2k5 preset  
 P2 = 2k2 linear  
 \*75  $\Omega$  = 150  $\Omega$  || 150  $\Omega$   
 \*\*see text

##### Capacitors:

C1, C4 = 100 n  
 C2, C3 = 10  $\mu$ /16 V  
 C5 ... C7 = 100  $\mu$ /16 V  
 C8 = 470  $\mu$ /35 V  
 C9 = 330 n

##### Semiconductors:

D1 = 1N4148  
 D2 ... D5 = 1N4001  
 T1 = BC 547B  
 T2 = BC 557B  
 T3 = BD 137/139  
 IC1 = 7812

##### Miscellaneous:

S1 = double pole mains switch

F1 = 100 mA slow blow fuse

Tr1 = 15 V, 0.8 A mains transformer

Heatsink for IC1

Case, approximate dimensions 120 x 65 x 65 mm

of which is shown in figure 2.

'Construction' is really only a matter of fitting everything correctly to the printed circuit board and soldering it there. However, there are a few points to note. When three outputs are in use voltage regulator IC1 has to work reasonably hard and because of this it needs to be mounted on a heatsink. The 75 ohm resistors (marked with an asterisk) are not standard E12 values. They actually consist of two 150 ohms connected in parallel.

Very little needs be said about mechanical construction for this project. Depending on circumstances, it could be built into the case of some existing equipment, or it could be mounted in a case of its own. The only important point is that the 'amplification' pot must be freely accessible.

