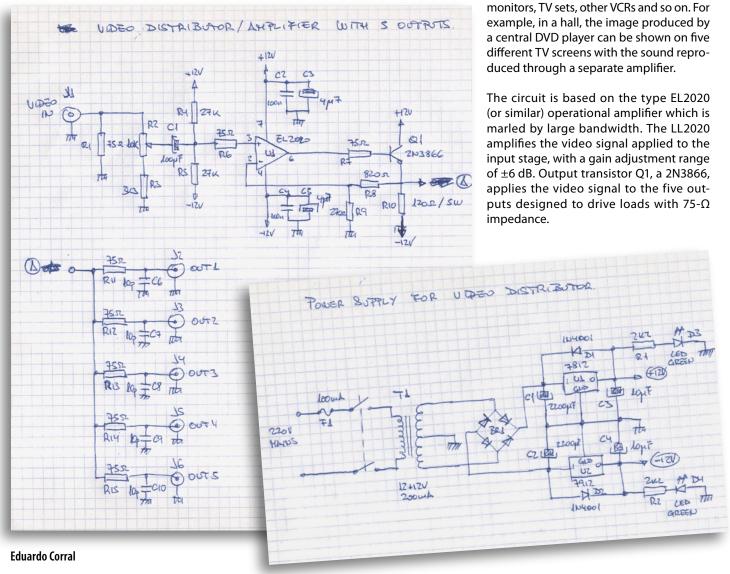
## **Five-output Video Distribution Amplifier**



Video fans and professionals in the field will find in this small signal distributor/amplifier an excellent ally when it's necessary to distribute a single video signal across several equipments. The circuit shown here should have a lot of applications.

Basically, the distribution amplifier takes the composite video signal from a video player (VCR) or a video generator (analogue output) and buffers it in such a way that it can be simultaneously applied to up to five different video equipment inputs, like The circuit requires a  $\pm 12$  V symmetrical supply voltage, which can be obtained from a conventional power supply as shown by the schematic.

(080478-I)